

# Boost Driver Debugging

Using Schoki's (v1) driver assembled by TA

13 Mar 2018











Original TA Driver  
*No modifications*

### Probe colours

V\_SW

V\_Out\_LED

V\_pot

V\_Input\_4.2

Low power input, notice that LED is 'flickering' as the MP34xx tries to generate a higher output voltage but quickly fails.



Original TA Driver  
*No modifications*

### Probe colours

V\_SW


V\_Out\_LED

V\_pot


V\_Input\_4.2

Zoom in from previous slide.

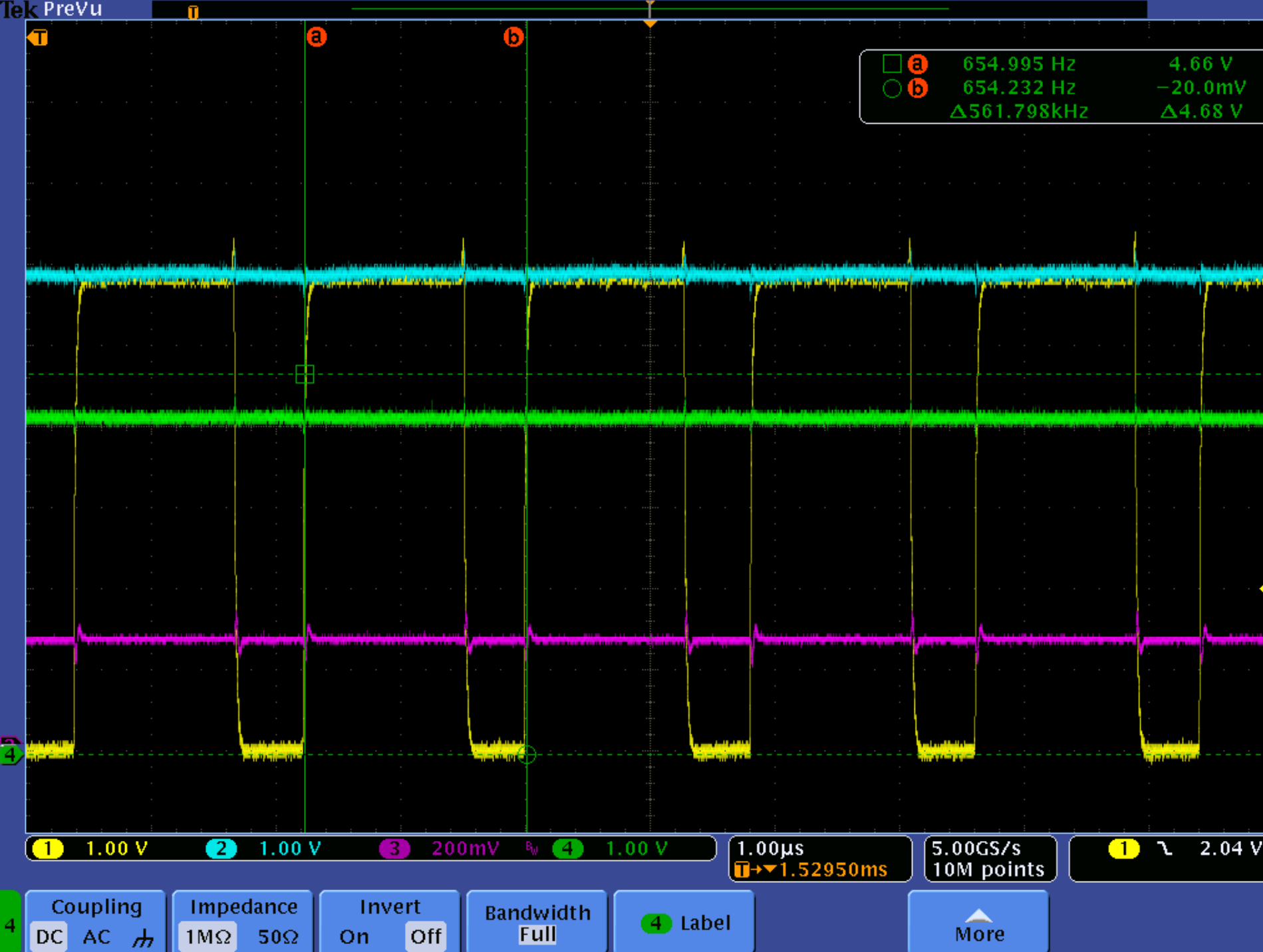Note the green input voltage. When the lower switch in the MP3431 turns on for a long duration,  $V_{in}$  drops significantly, causing the MP3431 to turn off and restart.





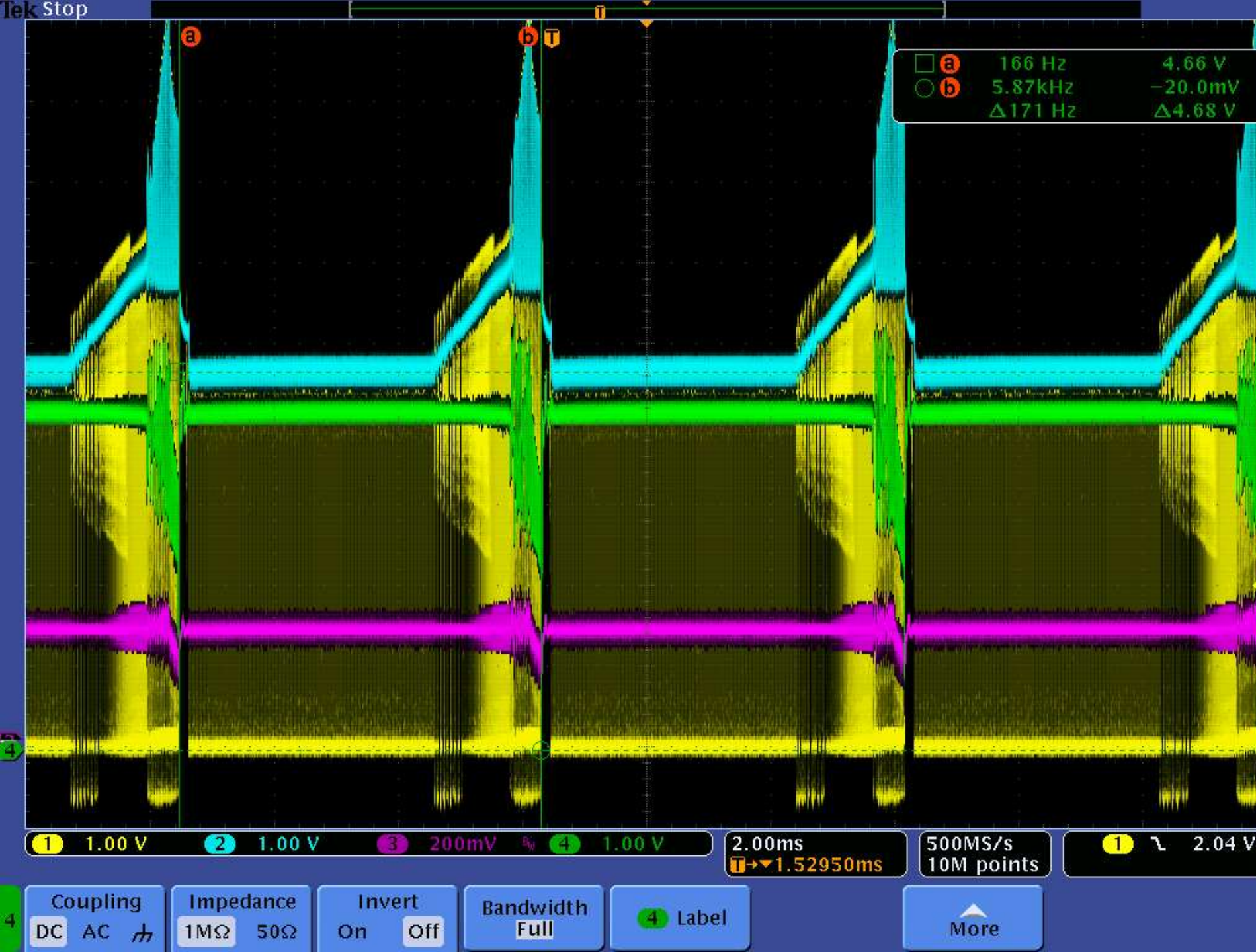

Original TA Driver

*Modified with extra 44uF  
of input capacitance*

**Probe colours**

V\_SW


V\_Out\_LED

V\_pot

V\_Input\_4.2

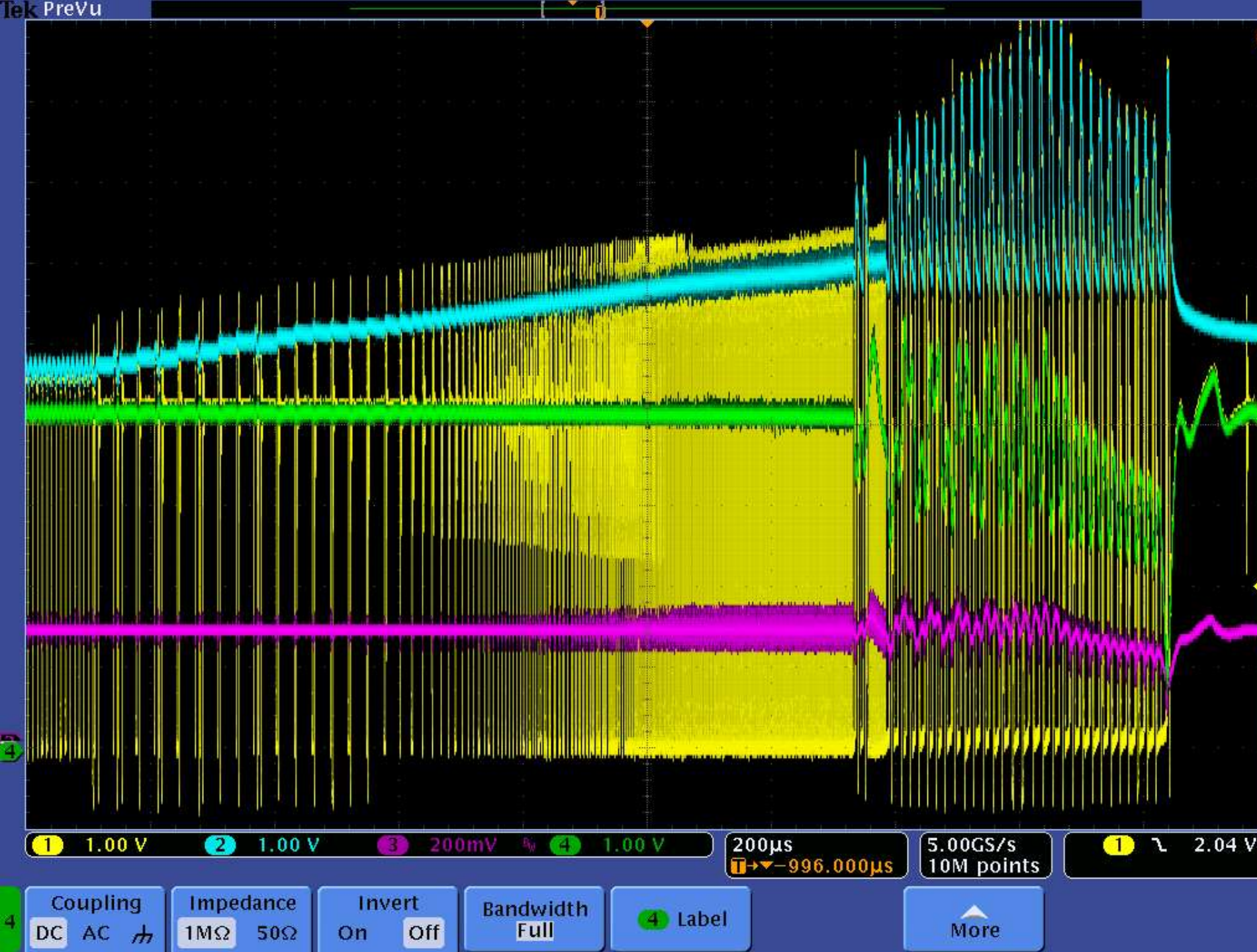In this problem  
configuration, LED begins  
flashing at  $\sim 170$  Hz. Let's see  
in more detail what's going  
on during each problem  
event.





Original TA Driver  
*Modified with extra 44uF  
of input capacitance*

### Probe colours

V\_SW

V\_Out\_LED

V\_pot

V\_Input\_4.2

Zoom in from previous chart.  
Note after startup phase,  
switching duty cycle  
increases based on SS, but at  
some point note how V\_in  
starts to drop and messes up  
the switching.



